

Chapter 3: Sequential Logic

Usage and Copyright Notice:

Copyright 2005 © Noam Nisan and Shimon Schocken

This presentation contains lecture materials that accompany the textbook “The Elements of Computing Systems” by Noam Nisan & Shimon Schocken, MIT Press, 2005.

The book web site, www.idc.ac.il/tecs , features 13 such presentations, one for each book chapter. Each presentation is designed to support about 3 hours of classroom or self-study instruction.

You are welcome to use or edit this presentation for instructional and non-commercial purposes.

If you use our materials, we will appreciate it if you will include in them a reference to the book’s web site.


And, if you have any comments, you can reach us at tecs.ta@gmail.com

Sequential VS combinational logic


- **Combinational devices:** operate on data only; provide calculation services (e.g. Nand ... ALU)
- **Sequential devices:** contain *state* and (optionally) operate on data; provide storage / synchronization services (e.g. flip-flop ... RAM)
- Sequential devices are clock-based; the clock cycles determine when the states are "committed"
- The low-level behavior of clocked / sequential gates is tricky
- The good news: the complex clock-dependency details can be encapsulated at a very elementary level in the computer's logic design.

Lecture plan

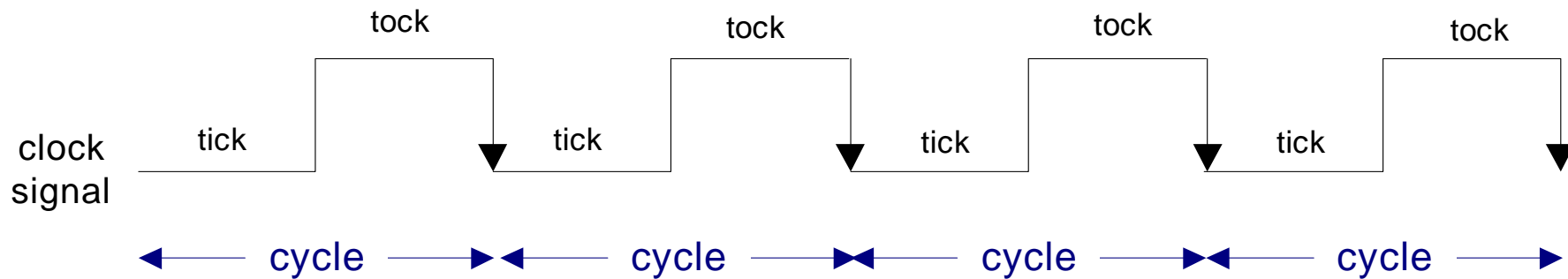- Clock
- A hierarchy of memory chips:
 - Flip-flop gates
 - Binary cells
 - Registers
 - RAM
- Counters
- Perspective.




 - In our jargon, a clock cycle = *tick*-phase (low), followed by a *tock*-phase (high)
- In real hardware, the clock is implemented by an oscillator
- In our hardware simulator, clock cycles can be simulated either
 - Manually, by the user, or
 - "Automatically," by a test script.



$$\text{out}(t) = \text{in}(t-1)$$



 
- A fundamental state-keeping device
- For now, let us not worry about the DFF *implementation*
- Memory devices are made from numerous flip-flops
- All regulated by the same master clock signal
- Notational convention:




1-bit register (Bit)

Objective: build a storage unit that can:

 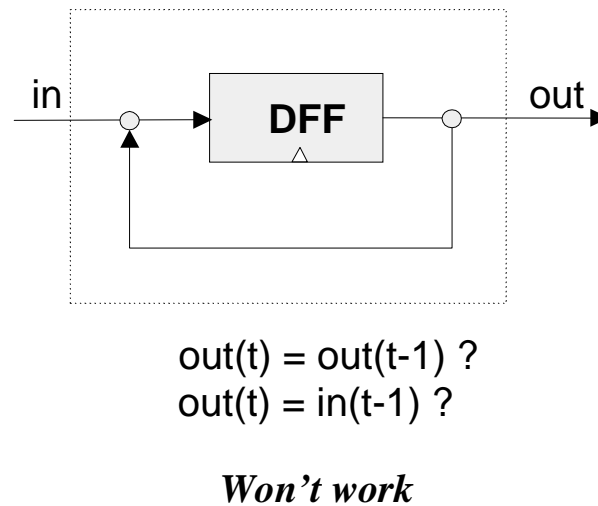 - (a) Change its state to a given input
- (b) Maintain its state over time (until changed)



 
if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)



if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)


OK

Interface

 


if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)

Implementation

 


- Load bit
- Read logic
- Write logic

 

if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)

1-bit register

 

if load(t-1) then out(t)=in(t-1)
else out(t)=out(t-1)

w-bit register

- Register's width: a trivial parameter
- Read logic
- Write logic

Aside: Hardware Simulation


HW
simulator
demo

HW simulator tutorial:

- Built-in chips
- Clocked chips
- GUI-empowered chips.


Random Access Memory (RAM)

HW
simulator
demo

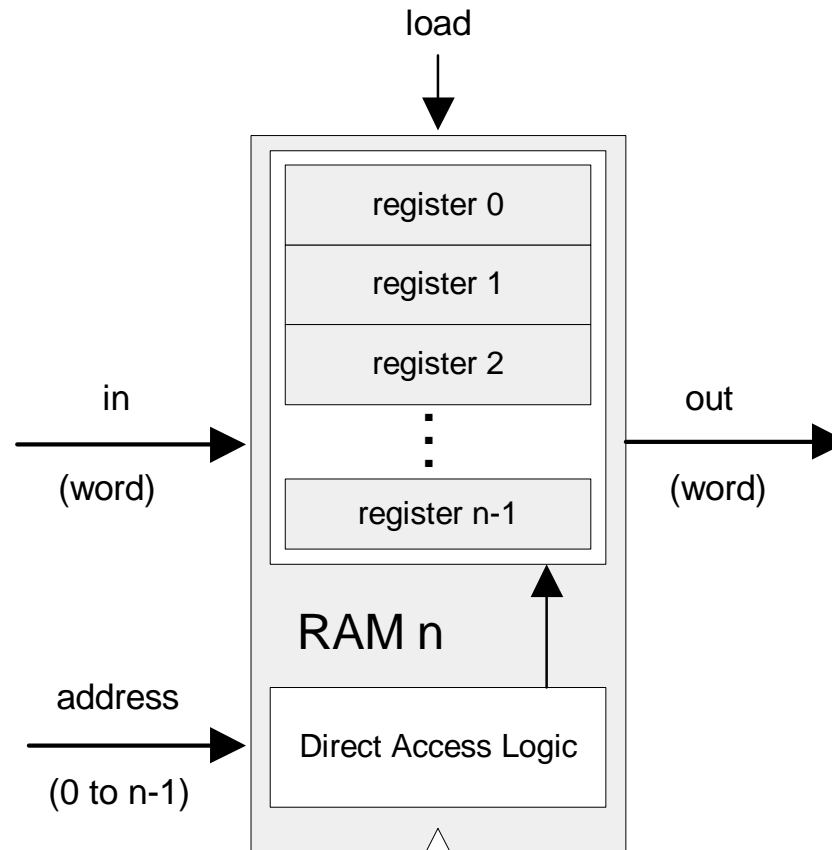

- Read logic
- Write logic.

RAM interface

 


```
Chip name: RAMn // n and k are listed below
Inputs:   in[16], address[k], load
Outputs:  out[16]
Function:  out(t) = RAM[address(t)](t)
          If load(t-1) then
              RAM[address(t-1)](t) = in(t-1)
Comment:  "=" is a 16-bit operation.
```

The specific RAM chips needed for the Hack platform are:

<u>Chip name</u>	<u>n</u>	<u>K</u>
RAM8	8	3
RAM64	64	6
RAM512	512	9
RAM4K	4096	12
RAM16K	16384	14

RAM anatomy

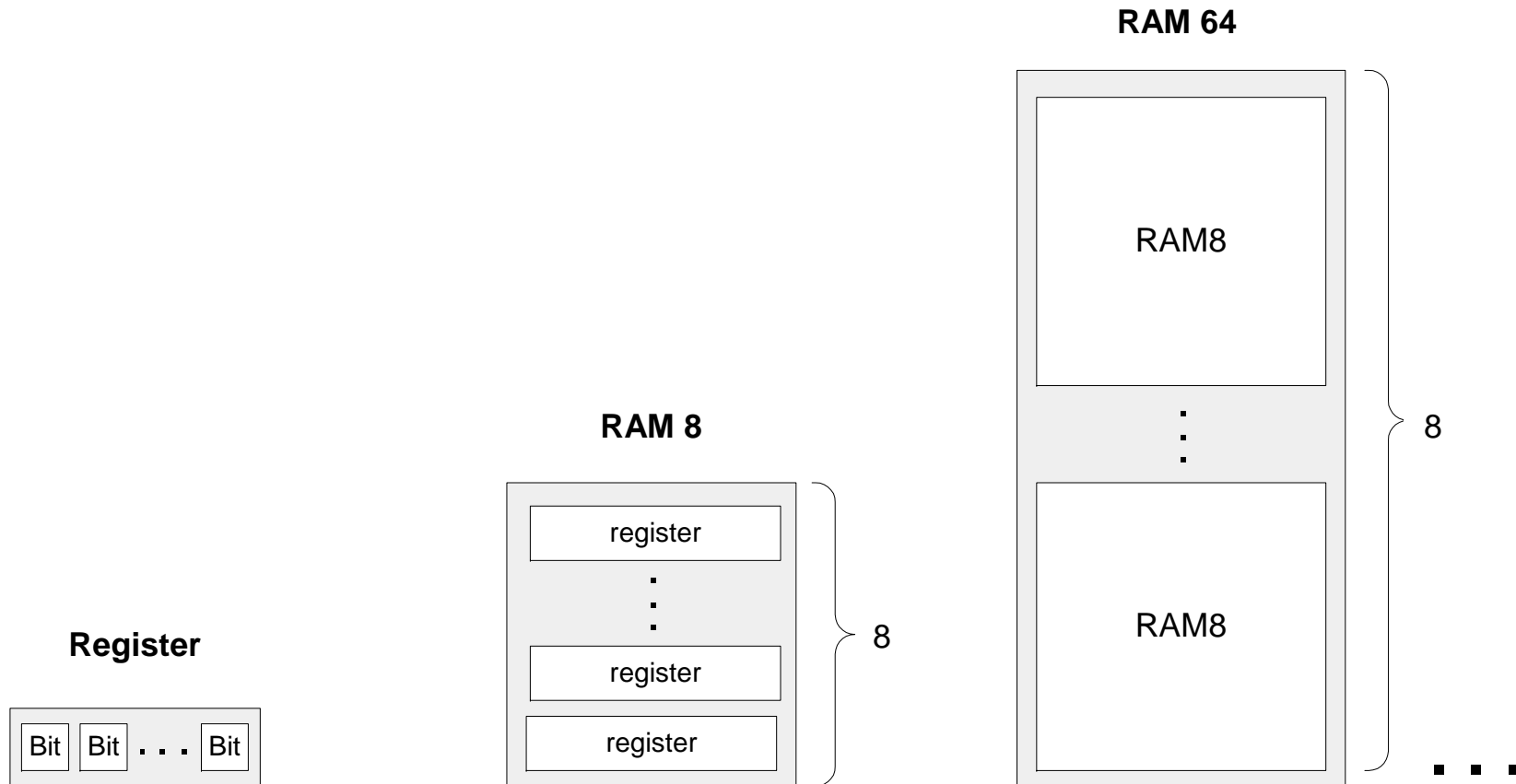


Historical aside: One of Intel's first RAM chips (c. 1972)



Counter

Needed: a storage device that can:

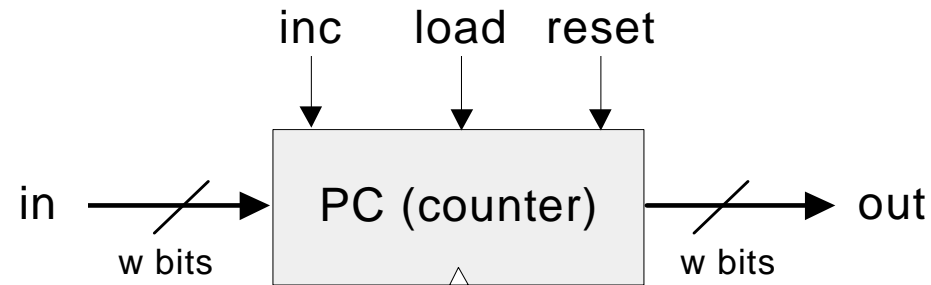- (a) set its state to some base value
- (b) increment the state in every clock cycle
- (c) maintain its state (stop incrementing) over clock cycles
- (d) reset its state




```
If reset(t-1) then out(t)=0
  else if load(t-1) then out(t)=in(t-1)
    else if inc(t-1) then out(t)=out(t-1)+1
      else out(t)=out(t-1)
```

- Typical function: *program counter*
- Implementation: register chip + some combinational logic.


Sequential VS combinational logic (revisited)

Combinational chip

 


$out = \text{some function of } (in)$

Sequential chip

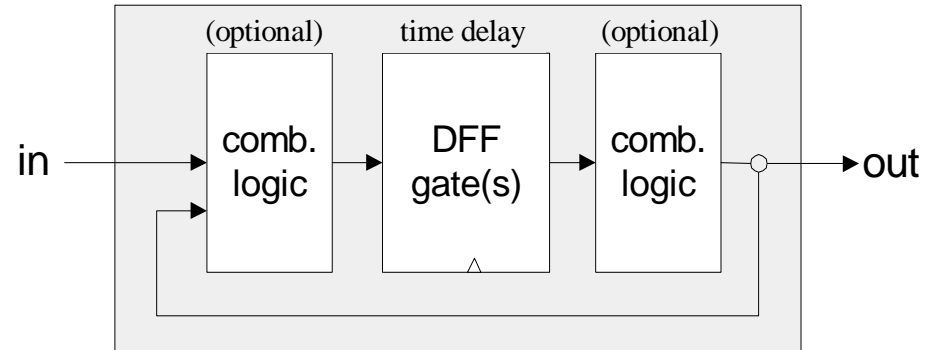


$out(t) = \text{some function of } (in(t-1), out(t-1))$

Time matters

 

 - During a tick-tock, the internal states of all the clocked chips are allowed to change, but their outputs are "latched"
- At the beginning of the next tick, the outputs of all the clocked chips in the architecture commit to the new values.



Implications:

- Challenge: propagation delays
- Solution: clock synchronization
- Cycle length and processing speed.

Perspective

- All the memory units described in this lecture are standard
- Typical memory hierarchy (listed in increasing access time and decreasing cost):
 - SRAM ("static"), typically used for the cache
 - DRAM ("dynamic"), typically used for main memory
 - Disk

(Elaborate caching / paging algorithms)
- A Flip-flop can be built from Nand gates
- But ... real memory units are highly optimized, using a great variety of storage technologies.